

# Computer Organization

## Lab 1: 32-bit ALU

Due: 2021/4/11

### 1. Goal

The goal of this LAB is to implement a 32-bit ALU (Arithmetic Logic Unit). ALU is the basic computing component of a CPU. Its operations include AND, OR, addition, subtraction, etc. This LAB will help you understand the CPU architecture. LAB 1 will be reused; you will use this module in later LABs. The function of testbench is to read input data automatically and output erroneous data. Please unzip the files in the same folder.

### 2. Homework Requirement

- a. Please use Xilinx Vivado or ModelSim as your HDL simulator. (Xilinx Vivado is preferred)
- b. Please **attach student IDs as comments** at the top of each file.
- c. Please zip the archive and **name it as "ID.zip"** (e.g., 08XXXXX.zip) before uploading to e3
- d. Testbench module is provided.
- e. Any work by fraud will absolutely get a zero point.**
- f. The names of top module and IO ports must be named as follows:

**Top module: alu.v**

```
module alu(  
    clk, // system clock (input)  
    rst_n, // negative reset (input)  
    src1, // 32 bits source 1 (input)  
    src2, // 32 bits source 2 (input)  
    ALU_control, // 4 bits ALU control input (input)  
    result, // 32 bits result (output)  
    zero, // 1 bit when the output is 0, zero must be set (output)  
    cout, // 1 bit carry out (output)  
    overflow // 1 bit overflow (output)  
);
```

ALU starts to work when the signal rst\_n is 1, and then catches the data from src1 and src2.

In order to have a good coding style, please obey the rules below:

- One module in one file.
- Module name and file name must be the same.

For example: The file "alu.v" only contains the module "alu".

**g. instruction set: basic operation instruction (60%)**

ALU Action	Name	ALU Control Input
And	And	0000
OR	Or	0001
Add	Addition	0010
Sub	Subtraction	0110
Nor	Nor	1100
Slt	Set less than	0111

**h. zcv three control signal: zero, carry out, overflow (30%)**


1. **“zero”** must be set when the result is 0.
2. **“cout”** must be set when there is a carry out.
3. **“overflow”** must be set when overflow.

**i. About alu\_top.v**

alu\_top.v is an 1-bit ALU module. We don't force you to use alu\_top.v to implement this homework. However, we still strongly recommend that you implement this homework by using alu\_top.v like the architecture diagram below. The design will become more complex in the following homework, so implementing your design by connecting multiple modules is an essential skill.

**Note:** You can add any module into your design if you want, but the top module must be alu in the alu.v defined in section f.

### 3. Architecture Diagram

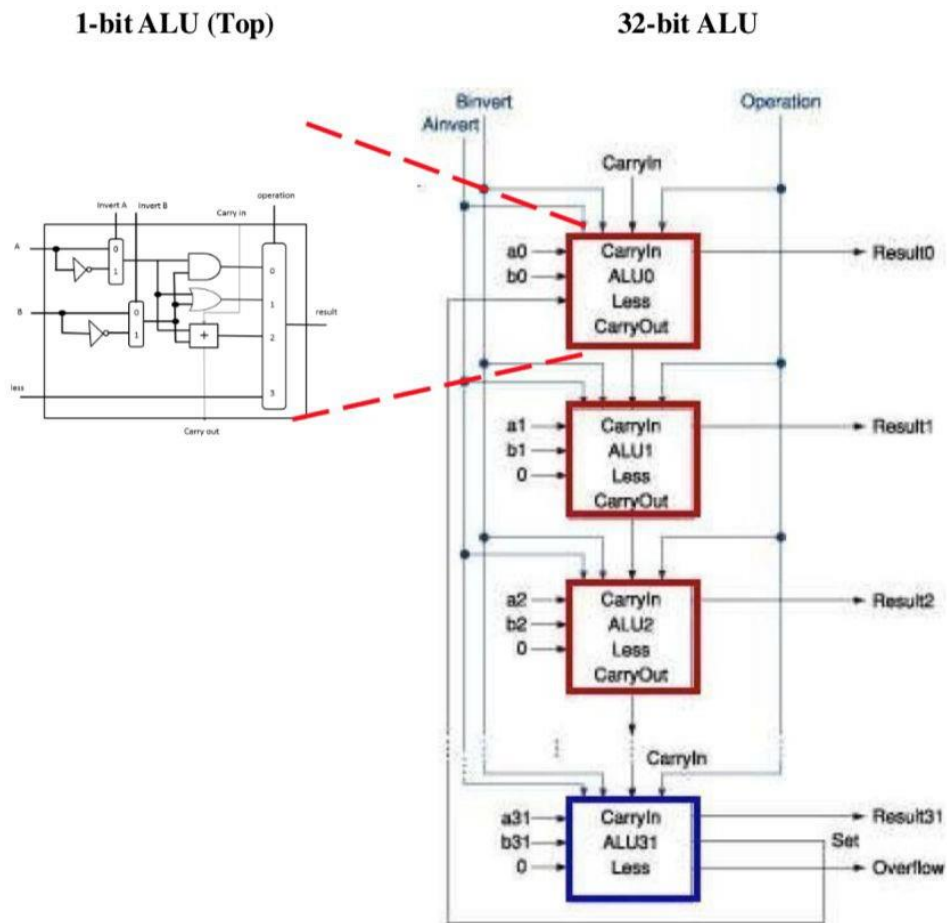

Blue frame is 1-bit ALU (Bottom)

### 4. Grade

- Total:**100 points (plagiarism will get 0 point)
- Report:** 10 points
- Late submission:** Score \* 0.8 before 4/18. After 4/18, you will get 0.


Please add all the .txt files into the project (please refer to section 5), after simulation finishes, you will get some information.

```
Simulator is doing circuit initialization process.
Finished circuit initialization process.
*****
Congratulation! All data are correct!
*****
```

## 5. Add Simulation Source

Before running simulation, you need to add testcases into your project.


### 1. Add sources

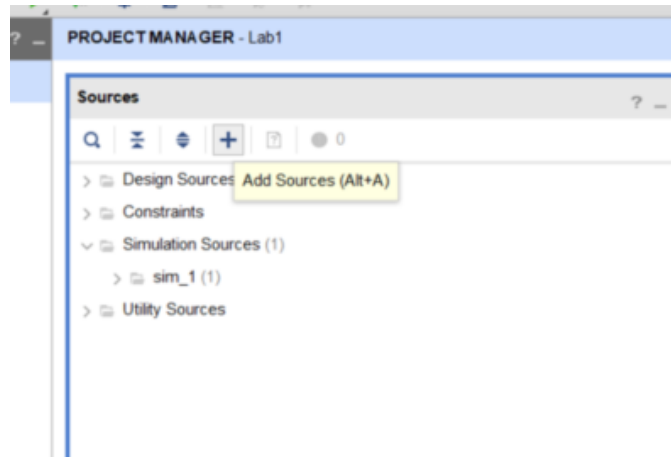


### 2. Add simulation sources



### 3. Add files

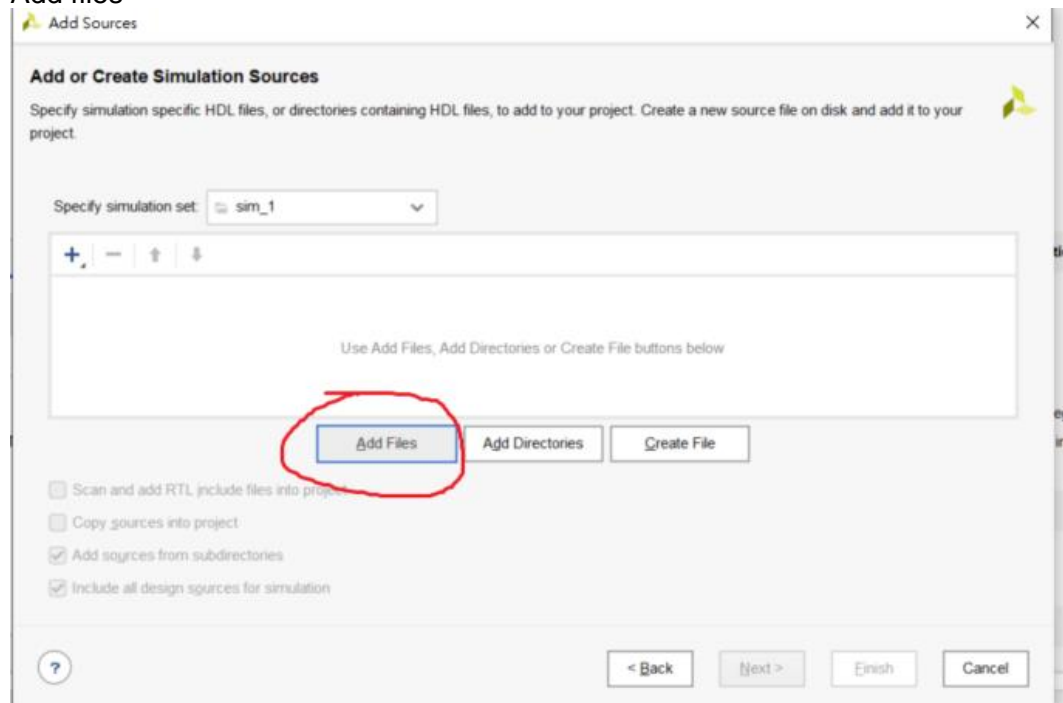
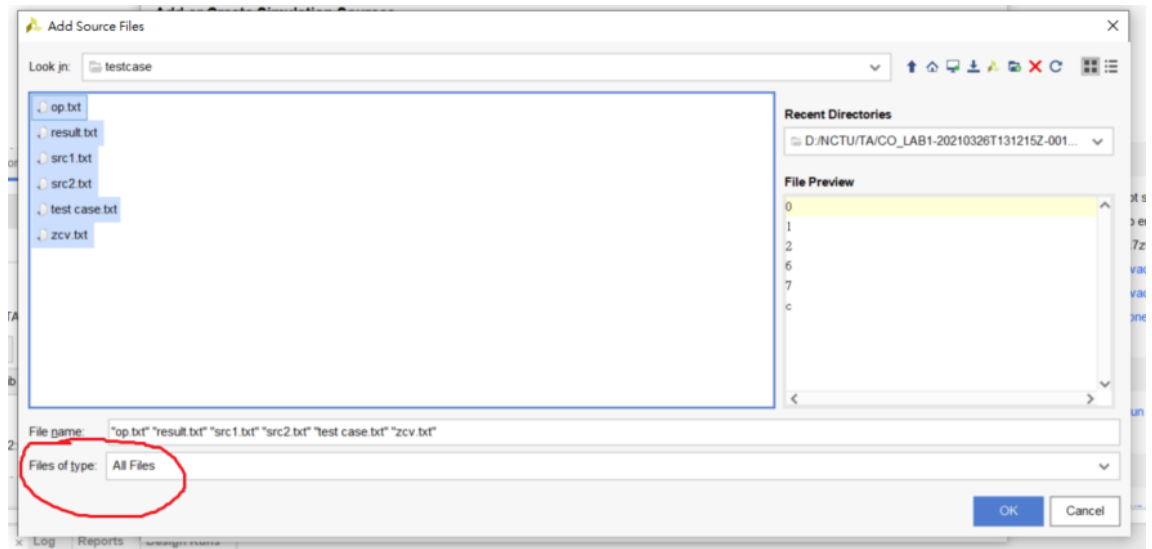
### 4. Add all files in testcase directory



## 5. Finish and start simulating

